

# Digital Design with the Verilog HDL

## Chapter 1: Digital Design Review


Binh Tran-Thanh

Department of Computer Engineering  
Faculty of Computer Science and Engineering  
Ho Chi Minh City University of Technology


January 15, 2024



# Technology Tradeoffs


 


# Design Methodology

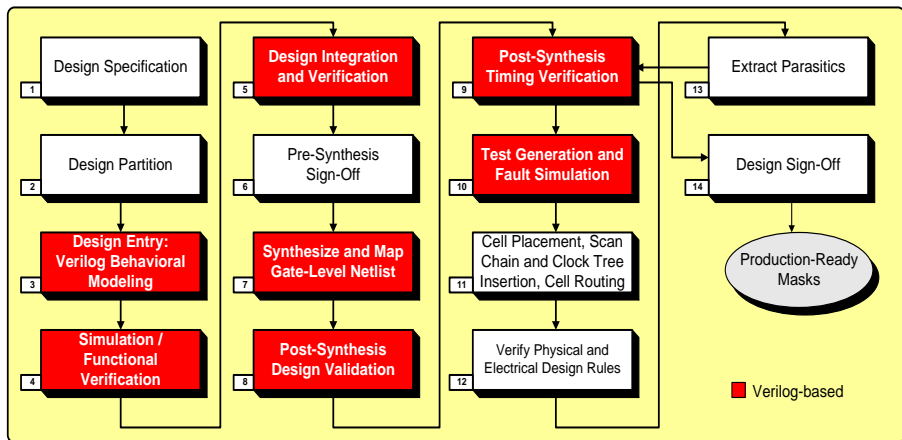


 
 
# Combinational – Sequential Logic

- Combinational logic:
  - The outputs at any time,  $t$ , are a function of only the inputs at time  $t$
- Sequential logic:
  - The outputs at time  $t$  are a function of the inputs at time  $t$  and **the outputs at time  $t-1$**






# Transistor

- nMos

  
 


- pMos

   

  
# CMOS Technology


- Complementary metal-oxide semiconductor
- Outputs are always either 0 or 1



Inverter

 

NAND gate


 


NOR gate





# Parallel and Serial

- nMOS: 1 = ON
- pMOS: 0 = ON

  


  - **Series:** all transistors are on
- **Parallel:** at least one transistor is on


 
# The “Conduction Complement” Rule



- CMOS gate’s output is always either 0 or 1
- For example: NAND
  - $Y=0$  if and only if both inputs are 1
  - $Y=1$  if and only if at least one input is 0
  - pMos transistors are parallel while nMos transistors are serial
- The “Conduction Complements” rule
  - The pull-up network always complements the pull-down network
  - **Parallel  $\rightarrow$  Serial, Serial  $\rightarrow$  Parallel**







# CMOS Inverter

A	Y
0	
1	

  



## CMOS Inverter

A	Y
0	1
1	

  



## CMOS Inverter

A	Y
0	1
1	0

  



# CMOS NAND Gate

A	B	Y
0	0	
0	1	
1	0	
1	1	

  



## CMOS NAND Gate

A	B	Y
0	0	1
0	1	
1	0	
1	1	

  



## CMOS NAND Gate

A	B	Y
0	0	1
<b>0</b>	<b>1</b>	<b>1</b>
1	0	
1	1	

  



## CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
<b>1</b>	<b>0</b>	<b>1</b>
1	1	

  

## CMOS NAND Gate



A	B	Y
0	0	1
0	1	1
1	0	1
<b>1</b>	<b>1</b>	<b>0</b>

  




## CMOS NOR Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

  
 
## 3-input NAND Gate


- Y is 0 if and only if ALL inputs are 1
- Y is 1 if and only if AT LEAST one input is 0



# Design CMOS Gates
 
## Example

Using the CMOS Technology, draw transistor structure of a 4-input NOR gate



# Design CMOS Gate (cont.)



## Example 2 (Homework)

Using the CMOS Technology, draw transistor structure of a 4-input NAND gate




 
 
# Compound Gates

Compound gates: can describe any inverter function (not function)


   
# Example: AOI22


$$Y = \overline{(A \bullet B) + (C \bullet D)}$$



## AOI22


Use AND/OR gate to implement?

- 20 transistors

 

## Example: O3AI


$$Y = \overline{(A + B + C)} \cdot D$$

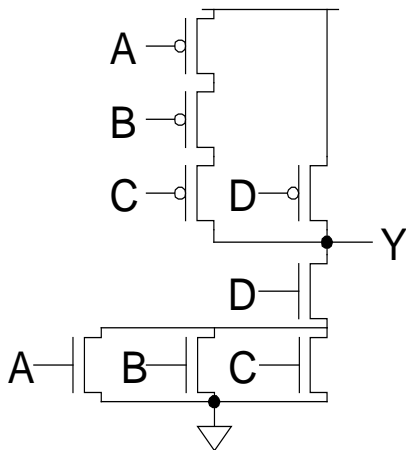


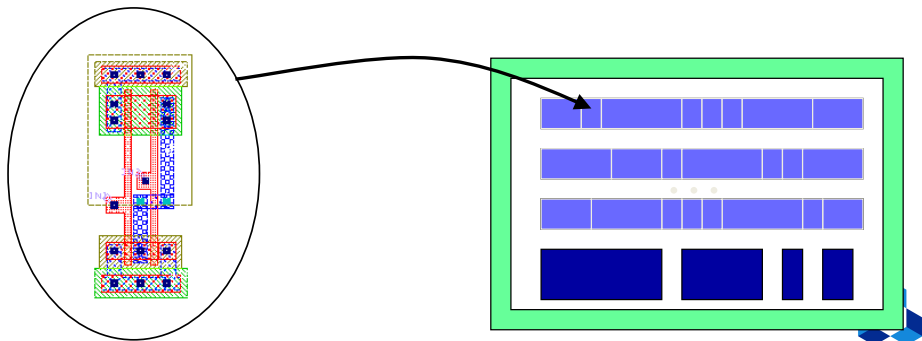
# Standard Cells

- Library of common gates and structures (cells)
- Decompose hardware in terms of these cells
- Arrange the cells on the chip
- Connect them using metal wiring



# FPGAs

- "Programmable" hardware
- Use small memories as truth tables of functions
- Decompose circuit into these blocks
- Connect using programmable routing
- SRAM bits control functionality

